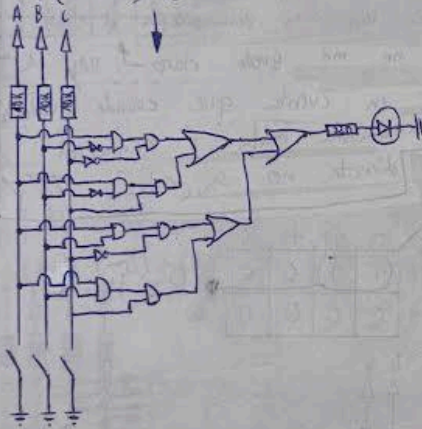


Logic gates Problems 4

A	B	C	S
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$S = (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C) + (A \cdot B \cdot \bar{C}) + (A \cdot B \cdot C)$$



A = Niebla densa = 1

B = Visibilidad inferior a 500m = 1

C = Radiolazo de avión encendido = 1

AB	00	01	11	10
0	0	0	1	1
1	0	0	1	1

$$S = A$$

